

# LAB 5 REPORT

Name – Chirath A.A.I.

Index – 210086E

Lab Task – The objective of this lab to design a 3-bit counter, program it to count both clockwise and counterclockwise dependent on an external input and test its operation in simulation and on the development board.

$Q_t$			Button	$Q_{t+1}$			$D_2$	$D_1$	$D_0$
$Q_2$	$Q_1$	$Q_0$		$Q_2$	$Q_1$	$Q_0$			
0	0	0	0	0	0	1	0	0	1
0	0	0	1	1	0	0	1	0	0
0	0	1	0	0	1	1	0	1	1
0	0	1	1	0	0	0	0	0	0
0	1	0	0	x	x	x	x	x	x
0	1	0	1	x	x	x	x	x	x
0	1	1	0	1	1	1	1	1	1
0	1	1	1	0	0	1	0	0	1
1	0	0	0	0	0	0	0	0	0
1	0	0	1	1	1	0	1	1	0
1	0	1	0	x	x	x	x	x	x
1	0	1	1	x	x	x	x	x	x
1	1	0	0	1	0	0	1	0	0
1	1	0	1	1	1	1	1	1	1
1	1	1	0	1	1	0	1	1	0
1	1	1	1	0	1	1	0	1	1

- $D_0$

$Q_2.Q_1 \backslash Q_0.B$	00	01	11	10
00	1			1
01	X	X	1	1
11		1	1	
10			X	X

$$D_0 = Q_1.B + Q_2'.B'$$

- $D_1$

$Q_2.Q_1 \backslash Q_0.B$	00	01	11	10
00				1
01	X	X		1
11		1	1	1
10		1	X	X

$$D_1 = Q_2.B + Q_0.B'$$

- $D_2$

$Q_2.Q_1 \backslash Q_0.B$	00	01	11	10
00		1		
01	X	X		1
11	1	1		1
10		1	X	X

$$D_2 = Q_1.B' + Q_0'.B$$

- VHDL codes

## D - Flip Flop

```

22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24
25 -- Uncomment the following library declaration if using
26 -- arithmetic functions with Signed or Unsigned values
27 --use IEEE.NUMERIC_STD.ALL;
28
29 -- Uncomment the following library declaration if instantiating
30 -- any Xilinx leaf cells in this code.
31 --library UNISIM;
32 --use UNISIM.VComponents.all;
33
34 entity D_FF is
35     Port ( D : in STD_LOGIC;
36           Res : in STD_LOGIC;
37           Clk : in STD_LOGIC;
38           Q : out STD_LOGIC;
39           Qbar : out STD_LOGIC);
40 end D_FF;
41
42 architecture Behavioral of D_FF is
43
44 begin
45
46     process (Clk) begin
47         if (rising_edge(Clk)) then
48             if Res = '1' then
49                 Q <= '0';
50                 Qbar <= '1';
51             else
52                 Q <= D;
53                 Qbar <= not D;
54             end if;
55         end if;
56     end process;
57
58 end Behavioral;

```

## Slow Clock

```

22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24
25 -- Uncomment the following library declaration if using
26 -- arithmetic functions with Signed or Unsigned values
27 --use IEEE.NUMERIC_STD.ALL;
28
29 -- Uncomment the following library declaration if instantiating
30 -- any Xilinx leaf cells in this code.
31 --library UNISIM;
32 --use UNISIM.VComponents.all;
33
34 entity Slow_Clk is
35     Port ( Clk_in : in STD_LOGIC;
36           Clk_out : out STD_LOGIC);
37 end Slow_Clk;
38
39 architecture Behavioral of Slow_Clk is
40
41     signal count : integer := 1;
42     signal clk_status : std_logic := '0';
43
44 begin
45     -- For 100 MHz input clock this generates 1 Hz clock
46     process (Clk_in) begin
47         if (rising_edge(Clk_in)) then
48             count <= count + 1;
49             if (count = 5) then
50                 clk_status <= NOT clk_status;
51                 Clk_out <= clk_status;
52                 count <= 1;
53             end if;
54         end if;
55     end process;
56
57 end Behavioral;


```

## Counter


```
22 library IEEE;
23 use IEEE.STD_LOGIC_1164.ALL;
24
25 -- Uncomment the following library declaration if using
26 -- arithmetic functions with Signed or Unsigned values
27 --use IEEE.NUMERIC_STD.ALL;
28
29 -- Uncomment the following library declaration if instantiating
30 -- any Xilinx leaf cells in this code.
31 --library UNISIM;
32 --use UNISIM.VComponents.all;
33
34 entity Counter is
35     Port ( Dir : in STD_LOGIC;
36           Res : in STD_LOGIC;
37           Clk : in STD_LOGIC;
38           Q : out STD_LOGIC_VECTOR (2 downto 0));
39 end Counter;
40
41 architecture Behavioral of Counter is
42
43     component D_FF port(
44         D : in STD_LOGIC;
45         Res : in STD_LOGIC;
46         Clk : in STD_LOGIC;
47         Q : out STD_LOGIC;
48         Qbar : out STD_LOGIC);
49     end component;
50
51     component Slow_Clk port(
52         Clk_in : in STD_LOGIC;
53         Clk_out : out STD_LOGIC);
54     end component;
55
56     signal D0, D1, D2 : STD_LOGIC; -- Internal signals
57     signal Q0, Q1, Q2 : STD_LOGIC; -- Internal signals
58     signal Clk_slow : STD_LOGIC; -- Internal clock
59
60     begin
61
62     Slow_Clk0 : Slow_Clk port map(
63         Clk_in => Clk,
64         Clk_out => Clk_slow);
65
66     D_FF0 : D_FF port map (
67         D => D0,
68         Res => Res,
69         Clk => Clk_slow,
70         Q => Q0);
71     D_FF1 : D_FF port map (
72         D => D1,
73         Res => Res,
74         Clk => Clk_slow,
75         Q => Q1);
76     D_FF2 : D_FF port map (
77         D => D2,
78         Res => Res,
79         Clk => Clk_slow,
80         Q => Q2);
81
82     D0 <= ((not Q2) and (not Dir)) or (Q1 and Dir);
83     D1 <= (Q0 and (not Dir)) or (Q2 and Dir);
84     D2 <= (Q1 and (not Dir)) or ((not Q0) and Dir);
85
86     Q(0) <= Q0;
87     Q(1) <= Q1;
88     Q(2) <= Q2;
89
90
91 end Behavioral;
```

- Timing Diagrams


## D - Flip Flop

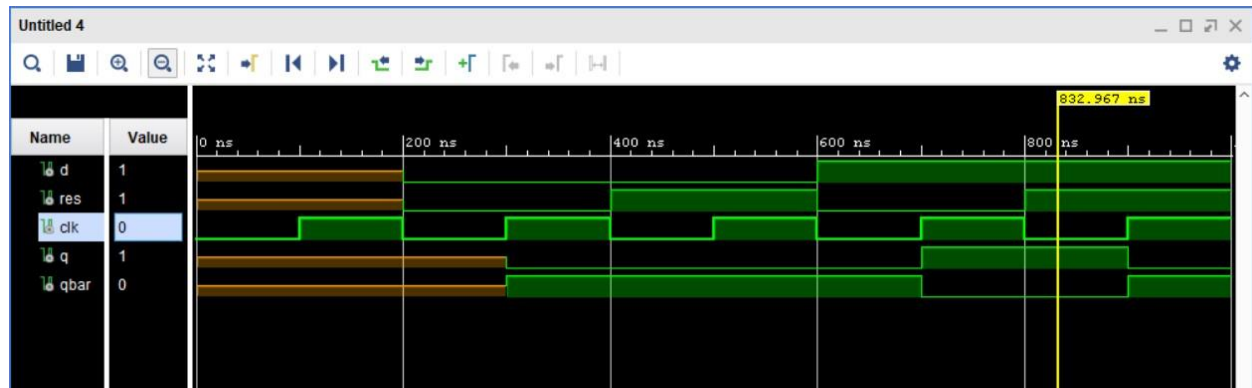

## Slow Clock

 

## Counter

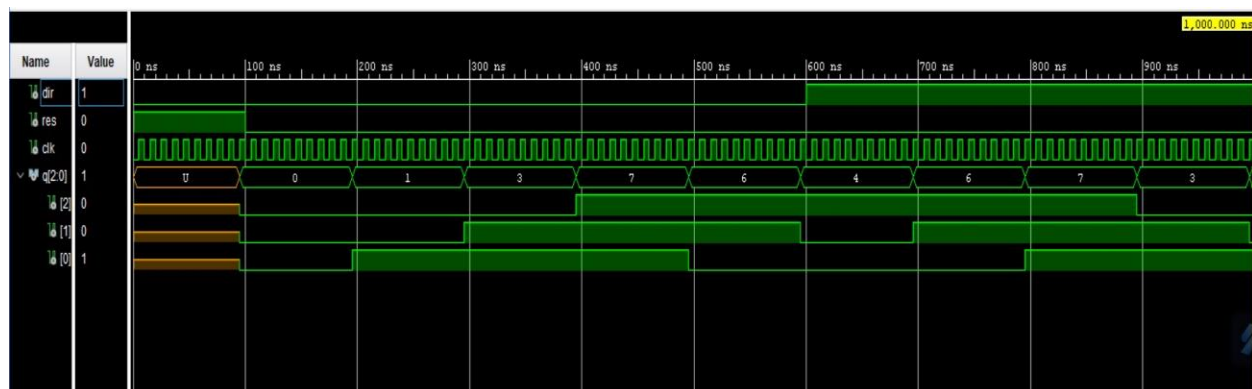

- Conclusion

In conclusion D – Flip flop is a essential component of digital circuits that can store one bit of information and it's commonly use in counters. D – flip flop is an improved version of S-R Flip flop.

On the other hand, counter is a digital circuit that sequentially count series of events and its made by series of D – Flip flops. In this lab we created a counter we can change the direction in this one using a switch. There are other type of counters and the all a used in many different scenarios.